 


1. The two inputs A and B are connected to an R-S latch via two AND gates as shown in the figure. If $A = 1$ and $B = 0$, the output $Q\bar{Q}$ is



(GATE-IN2017)

- (a) 00
- (b) 10
- (c) 01
- (d) 11