 


1. The two inputs A and B are connected to to an R-S latch via two AND gates as shown in the figure. If  $A = 1$  and  $B = 0$ , the output  $Q\bar{Q}$  is



- (a) 00
- (b) 10
- (c) 01
- (d) 11